 


Lecture 7: Logic design

- Binary digital logic circuits:
 - Two voltage levels (ground and supply voltage) for 0 and 1
 - Built from transistors used as on/off switches
 - Analog circuits not very suitable for generic computing
 - Digital logic with more than two states is not practical

Combinational logic: output depends only on the current inputs
(no memory of past inputs)




Sequential logic: output depends on the current inputs as well as
(some) previous inputs




Combinational logic circuits

 - Inverter (or NOT gate): 1 input and 1 output
“invert the input signal”



 
- AND gate: minimum 2 inputs and 1 output
“output 1 only if both inputs are 1”



Combinational logic circuits


- OR gate:

- “output 1 if at least one input is 1”

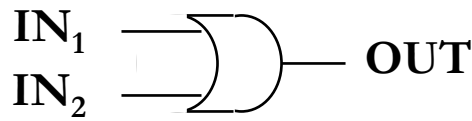	<table border="1"><thead><tr><th>IN₁</th><th>IN₂</th><th>OUT</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	IN ₁	IN ₂	OUT	0	0	0	0	1	1	1	0	1	1	1	1	$OUT = IN_1 + IN_2$
IN ₁	IN ₂	OUT															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

- NAND gate:

- “output 1 if both inputs are not 1” (NOT AND)

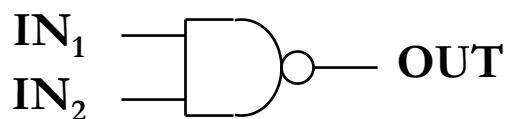	<table border="1"><thead><tr><th>IN₁</th><th>IN₂</th><th>OUT</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	IN ₁	IN ₂	OUT	0	0	1	0	1	1	1	0	1	1	1	0	$OUT = \overline{IN_1 \cdot IN_2}$
IN ₁	IN ₂	OUT															
0	0	1															
0	1	1															
1	0	1															
1	1	0															




Combinational logic circuits


- NOR gate:

“output 1 if no input is 1” (NOT OR)


IN ₁	IN ₂	OUT
0	0	1
0	1	0
1	0	0
1	1	0

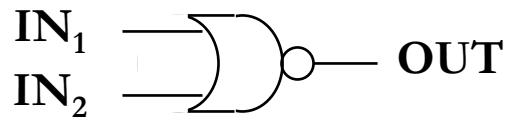 $OUT = \overline{IN_1 + IN_2}$

- Multiple-input gates:

 

OUT = 1 if all IN_i=1

 


OUT = 1 if any IN_i=1



Multiplexer

 - Multiplexer: a circuit for selecting one of many inputs



$$z = \begin{cases} i_0, & \text{if } c=0 \\ i_1, & \text{if } c=1 \end{cases}$$

c	i ₀	i ₁	z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


$$\begin{aligned} z &= \bar{c}.i_0.\bar{i}_1 + \bar{c}.i_0.i_1 + c.\bar{i}_0.i_1 + c.i_0.i_1 \\ &= \bar{c}.i_0.(\bar{i}_1 + i_1) + c.(\bar{i}_0 + i_0).i_1 \\ &= \bar{c}.i_0 + c.i_1 \end{aligned}$$

“sum of products form”



A multiplexer implementation

 
- Sum of products form: $i_1 \cdot c + i_0 \cdot \bar{c}$
 - Can be implemented with 1 inverter, 2 AND gates and 1 OR gate:



- Sum of products is not practical for circuits with large number of inputs (n)
 - The number of possible products can be proportional to 2^n


Arithmetic circuits

- 32-bit adder

 

64 inputs \rightarrow too complex for sum of products

- Full adder:

 

$$\text{sum} = \bar{a}.\bar{b}.c + \bar{a}.b.\bar{c} + a.\bar{b}.\bar{c} + a.b.c$$


$$\text{carry} = b.c + a.c + a.b$$

a	b	c	carry	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



Ripple carry adder

- 32-bit adder: chain of 32 full adders

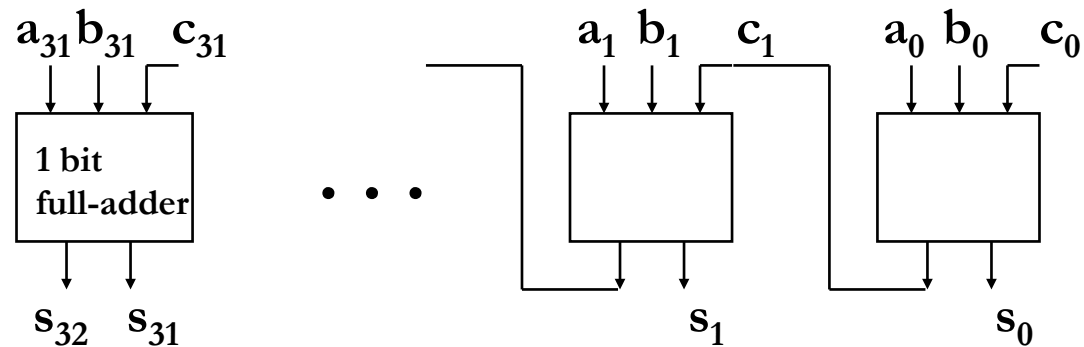

- Carry bits c_i are computed in sequence c_1, c_2, \dots, c_{32} (where $c_{32} = s_{32}$), as c_i depends on c_{i-1}
- Since sum bits s_i also depend on c_i , they too are computed in sequence




Propagation Delays

- Propagation delay = time delay between input signal change and output signal change at the other end
- Delay depends on technology (transistor, wire capacitance, etc.) and number of gates driven by the gate's output (**fan out**)
- e.g.: Sum of products circuits: 3 gate delays (inverter, AND, OR) → very fast!
- e.g.: 32-bit ripple carry adder: 65 gate delays (1 AND + 1 OR for each of 31 carries to propagate; 1 inverter + 1 AND + 1 OR for S_{31}) → slow



Sequential logic circuits

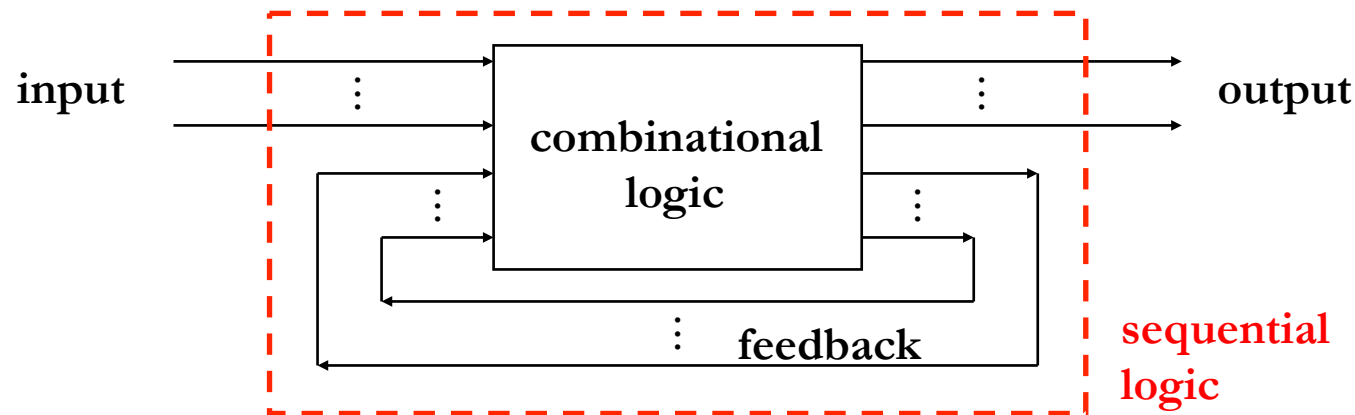

- Output depends on current inputs as well as past inputs
 - The circuit has memory
- Sequences of inputs generate sequences of outputs \Rightarrow sequential logic




Sequential logic circuits

- For a fixed input and n feedback signals, the circuit can have up to 2^n stable states
 - E.g. $n=1 \rightarrow$ one state if feedback signal = 0
one state if feedback signal = 1

 - Example: SR latch

- Inputs: R, S
- Feedback: q , \bar{q}
- Output: Q




SR Latch

■ Truth table:



S	R	Q_i
0	0	Q_{i-1}
0	1	0
1	0	1
1	1	u

u=unused

 

■ Usage: 1-bit memory

  
- Keep the value in memory by maintaining $S=0$ and $R=0$
- Set the value in memory to 0 (or 1) by setting $R=1$ (or $S=1$) for a short time



Timing of events


- Asynchronous sequential logic

 - State (and possibly output) of circuit changes whenever inputs change





- Synchronous sequential logic

 
- State (and possibly output) can only change at times synchronized to an external signal → the **clock**




D flip-flop

  

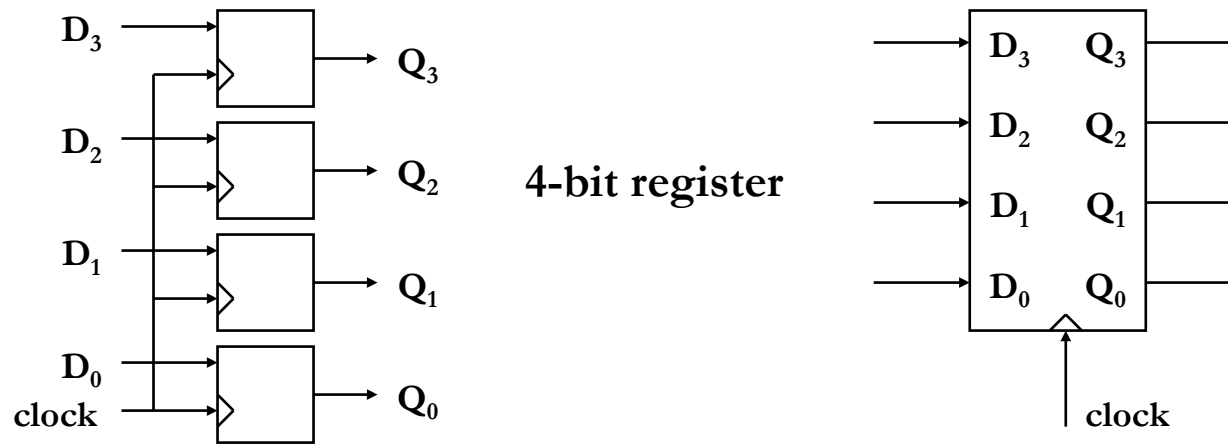- **Edge-triggered** flip-flop: on a +ve clock edge, D is copied to Q
- Can be used to build registers:



General sequential logic circuit

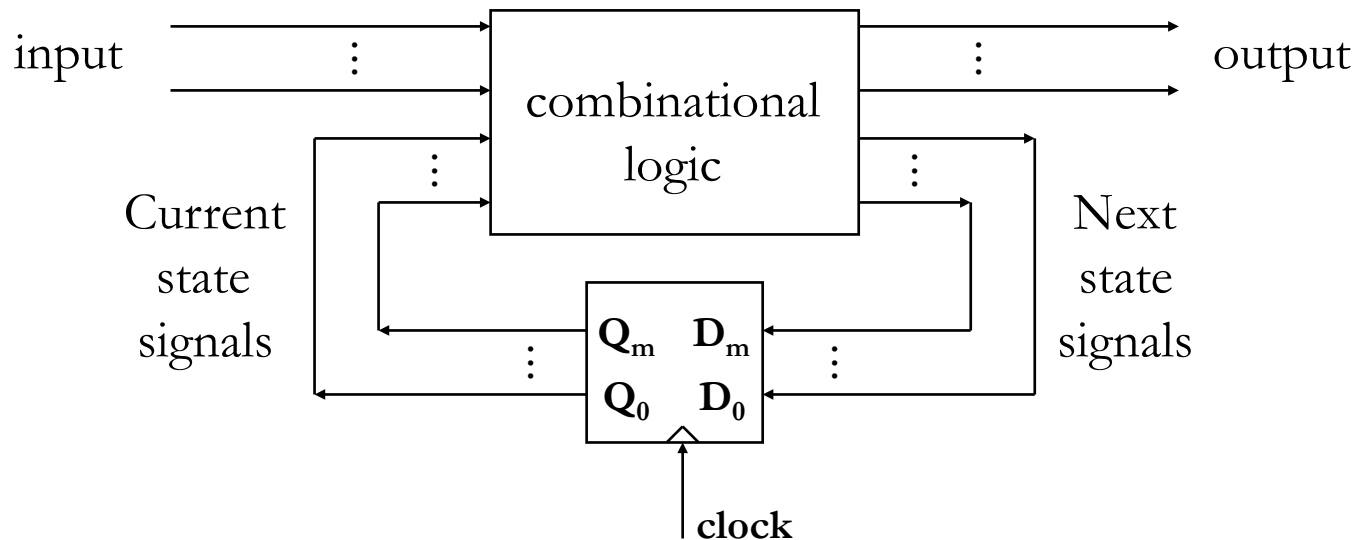


- Operation:
 - At every rising clock edge next state signals are propagated to current state signals
 - Current state signals plus inputs work through combinational logic and generate output and next state signals



Hardware FSM

 
- A sequential circuit is a (deterministic) Finite State Machine – FSM
- Example: Vending machine
 - Accepts 10p, 20p coins, sells one product costing 30p, no change given
 - Coin reader has 2 outputs: a,b for 10p, 20p coins respectively
 - Output z asserted when 30p or more has been paid in



FSM implementation

- Methodology:

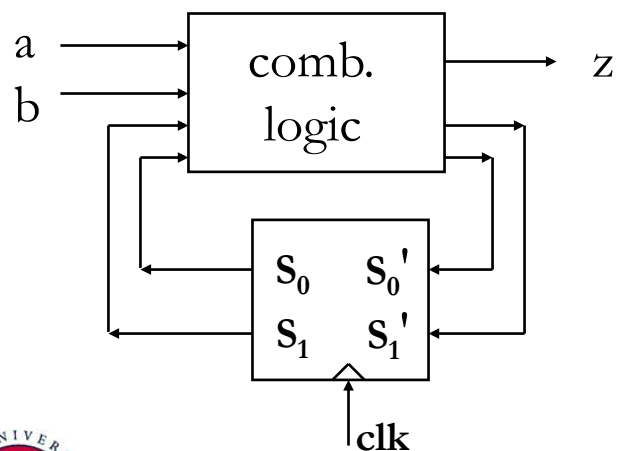- Choose encoding for states, e.g. $S_0=00, \dots, S_3=11$
- Build truth table for the next state s_1', s_0' and output z
- Generate logic equations for s_1', s_0', z
- Design comb logic from logic equations and add state-holding register



s_1	s_0	a	b	s_1'	s_0'	z
0	0	0	0	0	0	
0	0	0	1	1	0	0
0	0	1	0	0	1	
0	1	0	0	0	1	
0	1	0	1	1	1	0
0	1	1	0	1	0	

