 


## Lecture 7: Logic design

- Binary digital logic circuits:
  - Two voltage levels: 0 and 1 (ground and supply voltage)
  - Built from transistors used as on/off switches
  - Analog circuits not very suitable for generic computing
  - Digital logic with more than two states is not practical

**Combinational logic:** output depends only on the current inputs  
(no memory of past inputs)



**Sequential logic:** output depends on the current inputs as well as  
(some) previous inputs



 
## Combinational logic circuits

- Inverter (or NOT gate): 1 input and 1 output  
“invert the input signal”




- AND gate: minimum 2 inputs and 1 output  
“output 1 only if both inputs are 1”



## Combinational logic circuits

- OR gate:

- “output 1 if at least one input is 1”

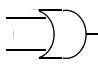
|        |   |       |
|--------|---|-------|
| $IN_1$ |  | $OUT$ |
| $IN_2$ |   |       |

| $IN_1$ | $IN_2$ | $OUT$ |
|--------|--------|-------|
| 0      | 0      | 0     |
| 0      | 1      | 1     |
| 1      | 0      | 1     |
| 1      | 1      | 1     |

$OUT = IN_1 + IN_2$

- NAND gate:

- “output 1 if both inputs are not 1” (NOT AND)
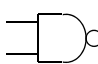
|        |   |       |
|--------|---|-------|
| $IN_1$ |  | $OUT$ |
| $IN_2$ |   |       |

| $IN_1$ | $IN_2$ | $OUT$ |
|--------|--------|-------|
| 0      | 0      | 1     |
| 0      | 1      | 1     |
| 1      | 0      | 1     |
| 1      | 1      | 0     |


$OUT = \overline{IN_1 \cdot IN_2}$



## Combinational logic circuits

- NOR gate:


- “output 1 if no input is 1” (NOT OR)
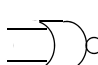
|        |   |       |
|--------|---|-------|
| $IN_1$ |  | $OUT$ |
| $IN_2$ |   |       |


| $IN_1$ | $IN_2$ | $OUT$ |
|--------|--------|-------|
| 0      | 0      | 1     |
| 0      | 1      | 0     |
| 1      | 0      | 0     |
| 1      | 1      | 0     |

$OUT = \overline{IN_1 + IN_2}$

- Multiple-input gates:

 

$OUT = 1$  if all  $IN_i = 1$

 


$OUT = 1$  if any  $IN_i = 1$


 
## Multiplexer

- Multiplexer: a circuit for selecting one of many inputs



$$z = \begin{cases} i_0, & \text{if } c=0 \\ i_1, & \text{if } c=1 \end{cases}$$

| $i_0$ | $i_1$ | $c$ | $z$ |
|-------|-------|-----|-----|
| 0     | 0     | 0   | 0   |
| 0     | 0     | 1   | 0   |
| 0     | 1     | 0   | 0   |
| 0     | 1     | 1   | 1   |
| 1     | 0     | 0   | 1   |
| 1     | 0     | 1   | 0   |
| 1     | 1     | 0   | 1   |
| 1     | 1     | 1   | 1   |


$$\begin{aligned} z &= \bar{i}_0 \cdot i_1 \cdot c + i_0 \cdot \bar{i}_1 \cdot \bar{c} + i_0 \cdot i_1 \cdot \bar{c} + i_0 \cdot i_1 \cdot c \\ &= \bar{i}_0 \cdot i_1 \cdot c + i_0 \cdot i_1 \cdot c + i_0 \cdot i_1 \cdot \bar{c} + i_0 \cdot \bar{i}_1 \cdot \bar{c} \\ &= (\bar{i}_0 + i_0) \cdot i_1 \cdot c + i_0 \cdot (\bar{i}_1 + i_1) \cdot \bar{c} \\ &= i_1 \cdot c + i_0 \cdot \bar{c} \end{aligned}$$

“sum of products form”


 
## A multiplexer implementation

- Sum of products form:  $i_1 \cdot c + i_0 \cdot \bar{c}$ 
  - Can be implemented with 1 inverter, 2 AND gates and 1 OR gate:




- Sum of products is not practical for circuits with large number of inputs ( $n$ )
  - Gates with more than 3 inputs are not practical to build
  - The number of possible products can be proportional to  $2^n$




## Arithmetic circuits

- 32-bit adder

 

64 inputs → too complex for sum of products

- Full adder:

 

$$\text{sum} = \bar{a}.\bar{b}.c + \bar{a}.b.\bar{c} + a.\bar{b}.\bar{c} + a.b.c$$


$$\text{carry} = b.c + a.c + a.b$$

| a | b | c | carry | sum |
|---|---|---|-------|-----|
| 0 | 0 | 0 | 0     | 0   |
| 0 | 0 | 1 | 0     | 1   |
| 0 | 1 | 0 | 0     | 1   |
| 0 | 1 | 1 | 1     | 0   |
| 1 | 0 | 0 | 0     | 1   |
| 1 | 0 | 1 | 1     | 0   |
| 1 | 1 | 0 | 1     | 0   |
| 1 | 1 | 1 | 1     | 1   |



## Ripple carry adder

- 32-bit adder: chain of 32 full adders

 

- Result bits ( $S_i$ ) are computed in sequence ( $S_0, S_1, \dots, S_{31}$ ) as  $S_i$  depends on  $C_i$ , which in turn requires  $S_{i-1}$  to be computed




## Propagation Delays

- Propagation delay = time delay between input signal arrival and output signal arrival at the other end
- Delay depends on technology (transistor, wire capacitance, etc.) and number of gates driven by the gate's output (**fan out**)
- e.g.: Sum of products circuits: 3 2-input gate delays (inverter, AND, OR) → very fast!
- e.g.: 32-bit ripple carry adder: 65 2-input gate delays (1 AND + 1 OR for each of 31 carries to propagate; 1 inverter + 1 AND + 1 OR for  $S_{31}$ ) → slow



## Sequential logic circuits

 

- Output depends on current inputs as well as past inputs
  - The circuit has memory
- Sequences of inputs generate sequences of outputs ⇒ **sequential logic**




## Sequential logic circuits

- For a fixed input and  $n$  feedback signals, the circuit can have  $2^n$  possible different behaviours (states)
  - E.g.  $n=1 \rightarrow$  one state if feedback signal = 0  
one state if feedback signal = 1

 - Example: SR latch


- Inputs: R, S
- Feedback:  $q$
- Output: Q



## SR Latch



- Truth table:

|          | S | R | $Q_i$     |
|----------|---|---|-----------|
|          | 0 | 0 | $Q_{i-1}$ |
|          | 0 | 1 | 0         |
| u=unused | 1 | 0 | 1         |
|          | 1 | 1 | u         |

 


- Usage: 1-bit memory

  - Keep the value in memory by maintaining  $S=0$  and  $R=0$
- Set the value in memory to 0 (or 1) by setting  $R=1$  (or  $S=1$ ) for a short time



 
# Timing of events



- Asynchronous sequential logic
  - State (and possibly output) of circuit changes whenever inputs change



 
- Synchronous sequential logic
  - State (and possibly output) can only change at times synchronized to an external signal → the **clock**




# D flip-flop

  

 - Edge-triggered flip-flop: on a clock edge D is copied to Q
- Can be used to build registers:



## General sequential logic circuit

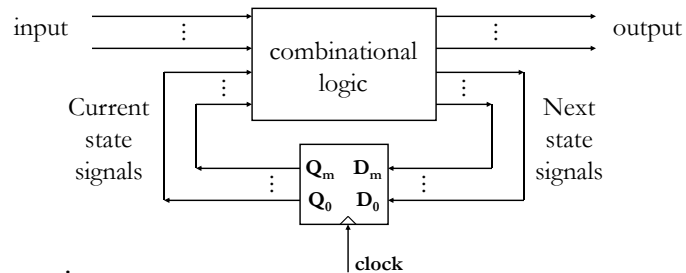


- Operation:
  - At every rising clock edge next state signals are propagated to current state signals
  - Current state signals plus inputs work through combinational logic and generate output and next state signals


 
## Hardware FSM


- A sequential circuit is a (deterministic) Finite State Machine – FSM
- Example: Vending machine
  - Accepts 10p, 20p coins, sells one product costing 30p, no change given
  - Coin reader has 2 outputs: a,b for 10p, 20p coins respectively
  - Output z asserted when 30p or more has been paid in




 
## FSM implementation

- Methodology:
  - Choose encoding for states, e.g  $S_0=00, \dots, S_3=11$
  - Build truth table for the next state  $s_1', s_0'$  and output  $z$
  - Generate logic equations for  $s_1', s_0', z$
  - Design comb logic from logic equations and add state-holding register



| $s_1$ | $s_0$ | a | b | $s_1'$ | $s_0'$ | z |
|-------|-------|---|---|--------|--------|---|
| 0     | 0     | 0 | 0 | 0      | 0      |   |
| 0     | 0     | 0 | 1 | 1      | 0      | 0 |
| 0     | 0     | 1 | 0 | 0      | 1      |   |
| 0     | 1     | 0 | 0 | 0      | 1      |   |
| 0     | 1     | 0 | 1 | 1      | 1      | 0 |
| 0     | 1     | 1 | 0 | 1      | 0      |   |

